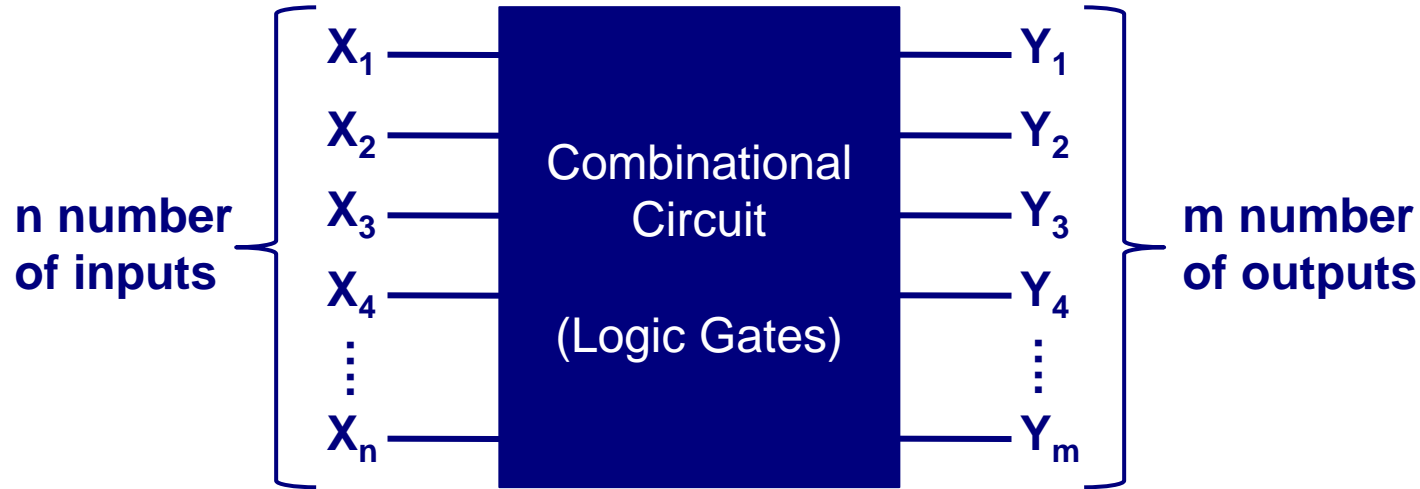




Combinational Circuits (Part-I)

Nilesh Patidar and Shiraz Husain



Combinational Circuits



Does not contain any memory element/feedback path

Half adder

  - Half adder is used for addition of 2 bits.



A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Handwritten annotations: A green bracket labeled "xor" is above the Sum column. A blue bracket labeled "and" is above the Carry column. A green line is drawn under the Sum column values.

Half adder

K-map for Sum

A \ B	B' (0)	B (1)
A' (0)	0 0	1 1
A (1)	1 2	0 3

difference


$$\begin{aligned}\text{Sum} &= AB' + A'B \\ &= A \oplus B\end{aligned}$$

K-map for Carry

A \ B	B' (0)	B (1)
A' (0)	0 0	0 1
A (1)	0 2	1 3

$$\text{Carry} = AB$$



Half adder

 

Logic Circuit of Half adder


Full adder

  - Full adder is used for addition of 3 bits.



			XOR	AND
A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full adder

 


$A \backslash BC$	$B'C' \text{ (00)}$	$B'C \text{ (01)}$	$BC \text{ (11)}$	$BC' \text{ (10)}$
$A' \text{ (0)}$	0 0	1 1	0 3	1 2
$A \text{ (1)}$	1 4	0 5	1 7	0 6

$$\begin{aligned}
 \text{Sum} &= AB'C' + ABC + A'B'C + A'BC' \\
 &= A(B'C' + BC) + A'(B'C + BC') \\
 &= A(B \oplus C)' + A'(B \oplus C) \\
 &= A \oplus B \oplus C
 \end{aligned}$$

FULL SUBTRACT


Full adder

 

$A \backslash BC$	$B'C' \text{ (00)}$	$B'C \text{ (01)}$	$BC \text{ (11)}$	$BC' \text{ (10)}$
$A' \text{ (0)}$	0 0	0 1	1 3	0 2
$A \text{ (1)}$	0 4	1 5	1 7	1 6

Carry = $AC + BC + AB$ A' =SUB.


Full adder

 

$A \backslash BC$	$B'C' \text{ (00)}$	$B'C \text{ (01)}$	$BC \text{ (11)}$	$BC' \text{ (10)}$
$A' \text{ (0)}$	0 0	0 1	1 3	0 2
$A \text{ (1)}$	0 4	1 5	1 7	1 6

$$\begin{aligned}\text{Carry} &= AB'C + A'BC + AB \\ &= (AB' + A'B)C + AB \\ &= (A \oplus B)C + AB\end{aligned}$$


Full adder

 

logic circuit of full adder



Design of Full adder using Half adders

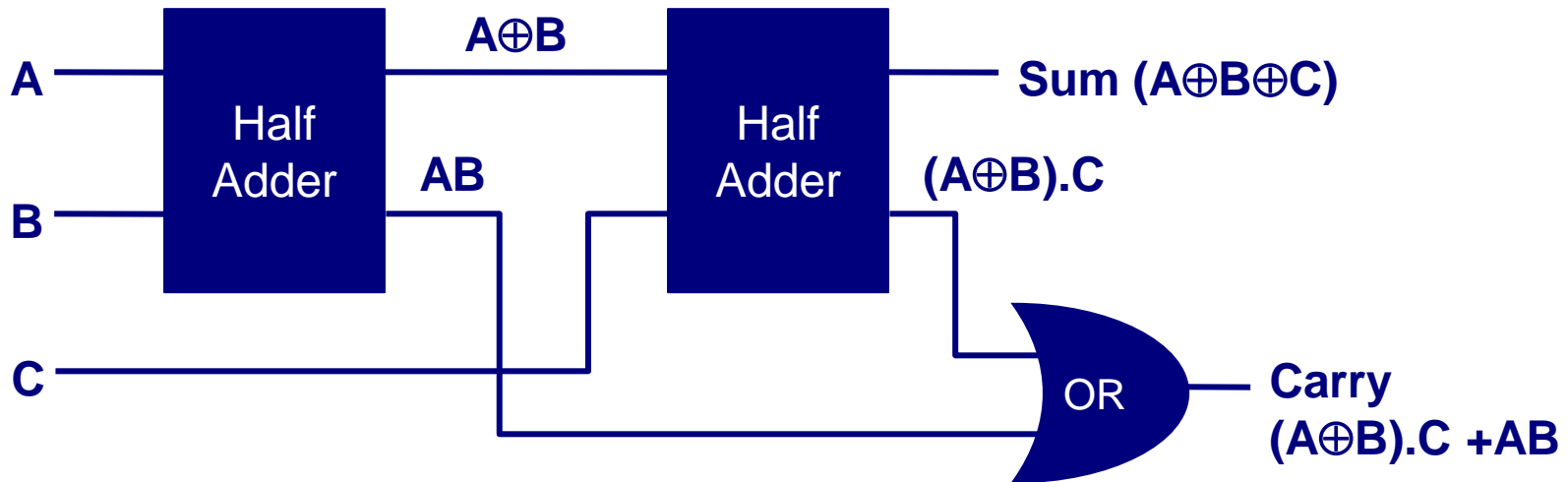- Full adder can be designed by using 2 half adders and 1 OR gate.



Half subtractor

  - Half subtractor is used for subtraction of 2 bits.



A	B	Difference	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Half subtractor

K-map for Difference

A \ B	B' (0)	B (1)
A' (0)	0	1
A (1)	1	0


$$\begin{aligned}\text{Difference} &= AB' + A'B \\ &= A \oplus B\end{aligned}$$

K-map for Borrow

A \ B	B' (0)	B (1)
A' (0)	0	1
A (1)	0	0

$$\text{Borrow} = A'B$$


Half subtractor

 

Logic Circuit of Half subtractor

Full subtractor

 
- Full subtractor is used for subtraction of 3 bits.



Truth Table

A	B	C	Difference	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


Full subtractor

 

$A \backslash BC$	$B'C' \text{ (00)}$	$B'C \text{ (01)}$	$BC \text{ (11)}$	$BC' \text{ (10)}$
$A' \text{ (0)}$	0 0	1 1	0 3	1 2
$A \text{ (1)}$	1 4	0 5	1 7	0 6

$$\begin{aligned}
 \text{Difference} &= AB'C' + ABC + A'B'C + A'BC' \\
 &= A(B'C' + BC) + A'(B'C + BC') \\
 &= A(B \oplus C)' + A'(B \oplus C) \\
 &= A \oplus B \oplus C
 \end{aligned}$$

Full subtractor

 

$A \backslash BC$	$B'C' (00)$	$B'C (01)$	$BC (11)$	$BC' (10)$
$A' (0)$	0	1	1	1
$A (1)$	0	0	1	0

$$\text{Borrow} = A'C + BC + A'B$$

Full subtractor



Q.1 Design the logic circuit of full subtractor by using logic gates from obtained Boolean equations from K-map.

Parallel Adder (4-bit)

- Example:

$$\begin{array}{r} C_4 C_3 C_2 C_1 \leftarrow \text{Initial Carry} \\ 0010 \\ + 1001 \leftarrow \text{Input A (A}_4\text{A}_3\text{A}_2\text{A}_1\text{)} \\ + 1101 \leftarrow \text{Input B (B}_4\text{B}_3\text{B}_2\text{B}_1\text{)} \\ \hline C_{\text{out}} \rightarrow 1 \boxed{0110} \leftarrow \text{Sum} \\ S_4 S_3 S_2 S_1 \end{array}$$

COMBINATIONAL




Serial Adder

SQUE....

- **Serial binary adder** is a logic circuit that performs the addition of **two binary numbers** in **serial form**. Serial binary adder performs bit by bit addition. Two shift **registers are used to store** the binary numbers that are to be added.
- A single full adder is used to add one pair of bits at a time along with the carry. The carry output from the full adder is applied to a D flip-flop. After that output is used as carry for next significant bits. The sum bit from the output of the full adder can be transferred into a third shift register.

Serial Adder

 


Sequential Circuit
because it contains
memory elements

Is it a combinational or sequential circuits?

BCD Adder

0110+

 - BCD stand for binary coded decimal. (Range from 0 to 9)



Maximum value of any BCD numbers is 9. So, maximum sum of two BCD numbers are 18 (without any carry) and 19 (in case of previous carry)

$$\text{BCD Sum} = 9 + 9 + 1(\text{carry}) = 19$$

BCD Adder

- Example: Add two BCD numbers.

$$\begin{array}{rcl} & 1\ 0\ 0\ 1 & \leftarrow 9 \text{ (in BCD)} \\ + & 0\ 1\ 0\ 1 & \leftarrow 5 \text{ (in BCD)} \\ \hline \text{Binary Sum} & 1\ 1\ 1\ 0 & \leftarrow 14 \text{ (in Decimal)} \\ & +\ 0\ 1\ 1\ 0 & \leftarrow \text{add 6 (in case of sum} > 9) \\ \hline \text{BCD Sum} & 0\ 0\ 0\ 1\ 0\ 1\ 0\ 0 & \leftarrow 1\ 4 \text{ (in BCD)} \end{array}$$

BCD Adder

Decimal	Binary Sum					BCD Sum				
	C'	S3'	S2'	S1'	S0'	C	S3	S2	S1	S0
0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	1	0	0	0	0	1
2	0	0	0	1	0	0	0	0	1	0
3	0	0	0	1	1	0	0	0	1	1
4	0	0	1	0	0	0	0	1	0	0
5	0	0	1	0	1	0	0	1	0	1
6	0	0	1	1	0	0	0	1	1	0
7	0	0	1	1	1	0	0	1	1	1
8	0	1	0	0	0	0	1	0	0	0
9	0	1	0	0	1	0	1	0	0	1
10	0	1	0	1	0	1	0	0	0	0
11	0	1	0	1	1	1	0	0	0	1
12	0	1	1	0	0	1	0	0	1	0
13	0	1	1	0	1	1	0	0	1	1
14	0	1	1	1	0	1	0	1	0	0
15	0	1	1	1	1	1	0	1	0	1
16	1	0	0	0	0	1	0	1	1	0
17	1	0	0	0	1	1	0	1	1	1
18	1	0	0	1	0	1	1	0	0	0
19	1	0	0	1	1	1	1	0	0	1

BCD Adder

We are adding “0110” (=6) only to the second half of the table.

The conditions are:


- If $C' = 1$ (Satisfies 16-19)
- If $S3'.S2' = 1$ (Satisfies 12-15)
- If $S3'.S1' = 1$ (Satisfies 10 and 11)

■ So, our logic is


$$C' + S3'.S2' + S3'.S1' = 1 \text{ (used to generate 6)}$$

BCD Adder (Implementation)


$$C' + S3'.S2' + S3'.S1' = 1$$

 


Multiplexer (MUX)

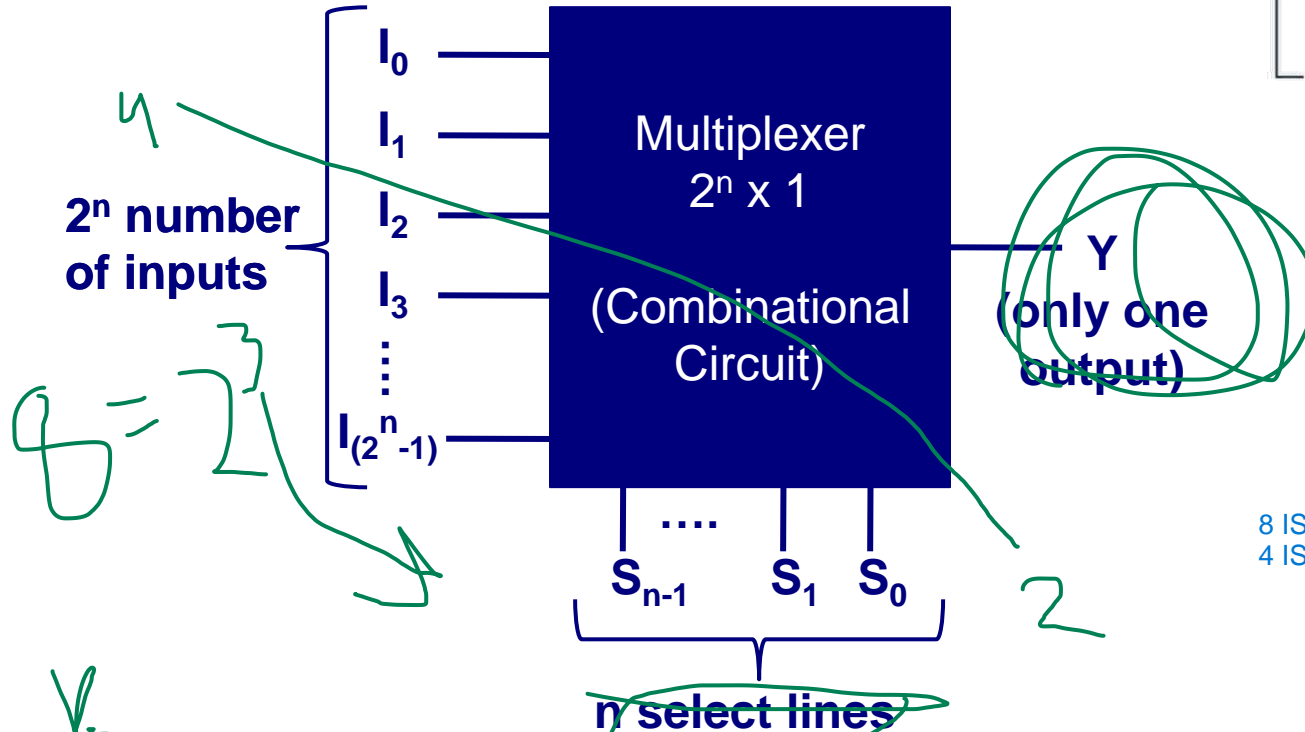

It is also called Data Selector


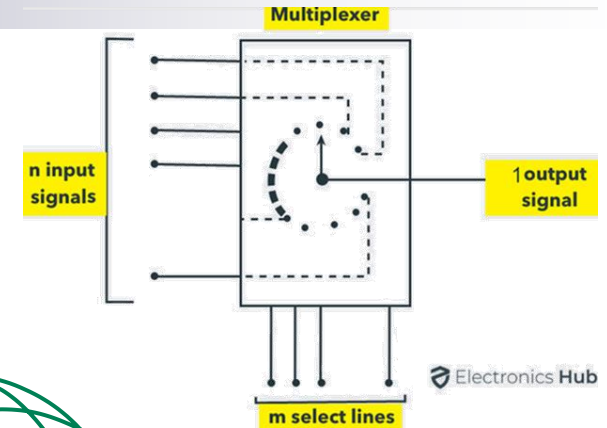


8 IS 1
4 IS 1

 


Symbolic
Representation

2x1 Multiplexer

  

S	Y
0	I_0
1	I_1

 

S	I_0	I_1	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$Y = S'I_0 + SI_1$$

$$S'I_0 + SI_1 = Y$$

$$Y = S'I_0 + SI_1$$


2x1 Multiplexer

K-map
for
2x1 MUX

$s \backslash I_0 I_1$	$I_0' I_1'$ (00)	$I_0' I_1$ (01)	$I_0 I_1$ (11)	$I_0 I_1'$ (10)
s' (0)	0	0	1	1
s (1)	0	1	1	0



$$Y = S'I_0 + SI_1$$

2x1 Multiplexer

 

$$Y = S'I_0 + SI_1$$


4x1 Multiplexer

  

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3


$$Y = S_1'S_0'I_0 + S_1'S_0I_1 + S_1S_0'I_2 + S_1S_0I_3$$

4x1 Multiplexer

 

$$Y = S_1'S_0'I_0 + S_1'S_0I_1 + S_1S_0'I_2 + S_1S_0I_3$$

4x1 MUX using 2x1 MUX

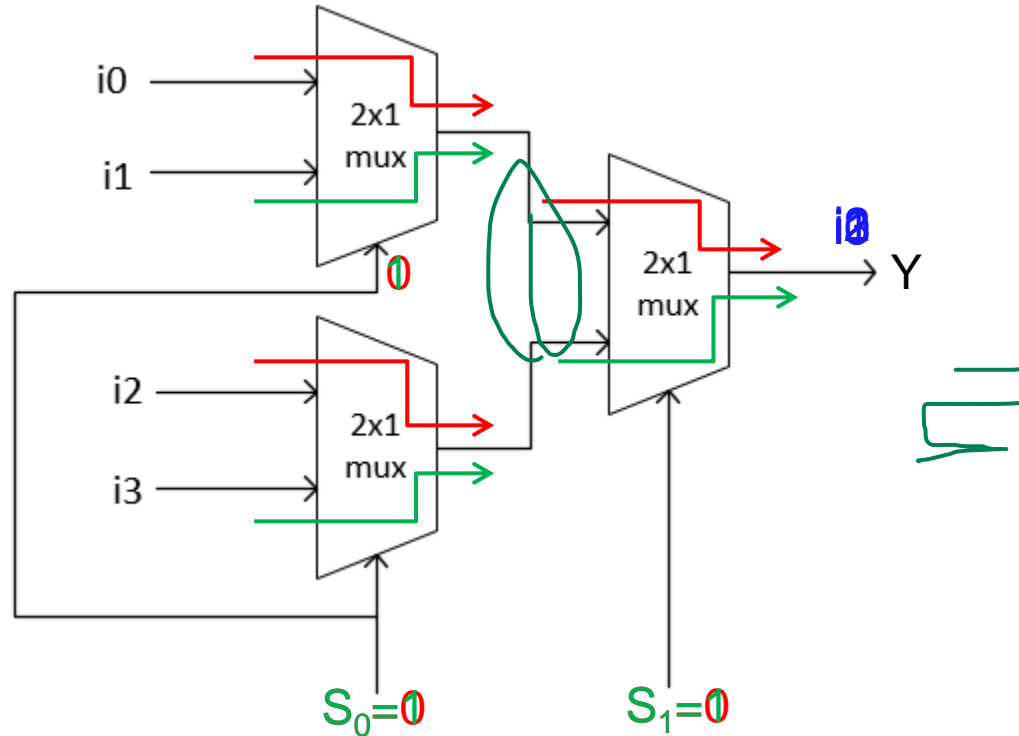

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

To implement $2^n \times 1$ MUX using 2×1 MUX, the total number of 2×1 MUX required is $(2^n - 1)$.

\therefore The number of 2×1 multiplexer required to implement 16×1 MUX will be:

$$n = 16 - 1 = 15$$

Or we can follow the below steps to calculate the same:

$$1^{\text{st}} \text{ stage} = \frac{16}{2} = 8$$

$$2^{\text{nd}} \text{ stage} = \frac{8}{2} = 4$$

$$3^{\text{rd}} \text{ stage} = \frac{4}{2} = 2$$

$$4^{\text{th}} \text{ stage} = \frac{2}{2} = 1$$


The sum will give the total number of MUX required to implement 16×1 multiplexer using 2×1 , i.e.

$$n = 8 + 4 + 2 + 1 = 15$$



Given MUX	To be implemented	Required
2 : 1	16 : 1	$8 + 4 + 2 + 1 = 15$
4 : 1	16 : 1	$4 + 1 = 5$
4 : 1	64 : 1	$18 + 4 + 1 = 21$
8 : 1	64 : 1	$8 + 1 = 9$
8 : 1	256 : 1	$32 + 4 + 1 = 37$

8x1 Multiplexer

8 is 1 using 4:1


 


De-Multiplexer (De-MUX)

 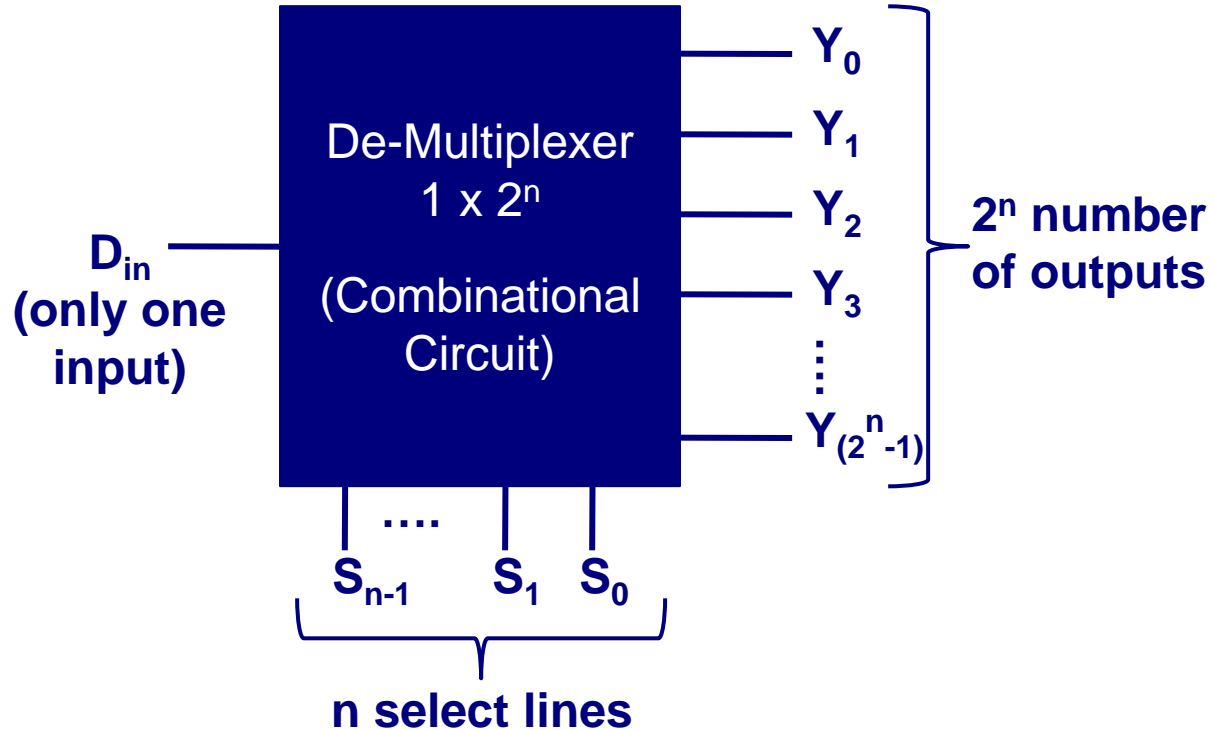


Symbolic Representation

1x2 De-Multiplexer

  

S	Y_0	Y_1
0	D_{in}	0
1	0	D_{in}

 


S	D_{in}	Y_0	Y_1
0	0	0	0
0	1	1	0
1	0	0	0
1	1	0	1



$$Y_0 = S'D_{in}$$

$$Y_1 = SD_{in}$$

1x2 De-Multiplexer

 

1x4 De-Multiplexer

 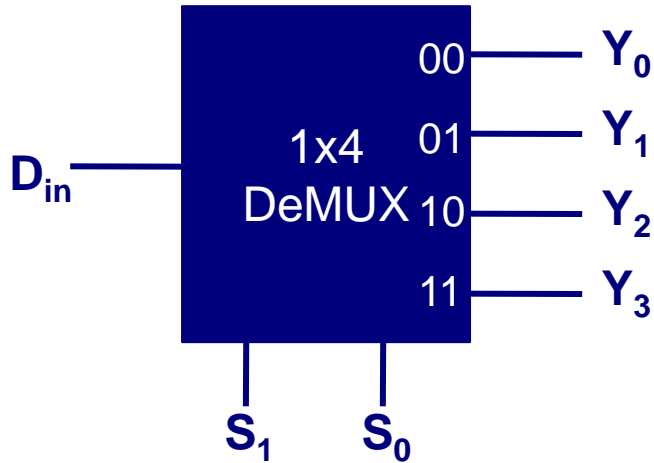

S_1	S_0	Y_0	Y_1	Y_2	Y_3
0	0	D_{in}	0	0	0
0	1	0	D_{in}	0	0
1	0	0	0	D_{in}	0
1	1	0	0	0	D_{in}


$$Y_0 = S_1' S_0' D_{in}$$

$$Y_2 = S_1 S_0' D_{in}$$

$$Y_1 = S_1' S_0 D_{in}$$

$$Y_3 = S_1 S_0 D_{in}$$

1x4 De-Multiplexer

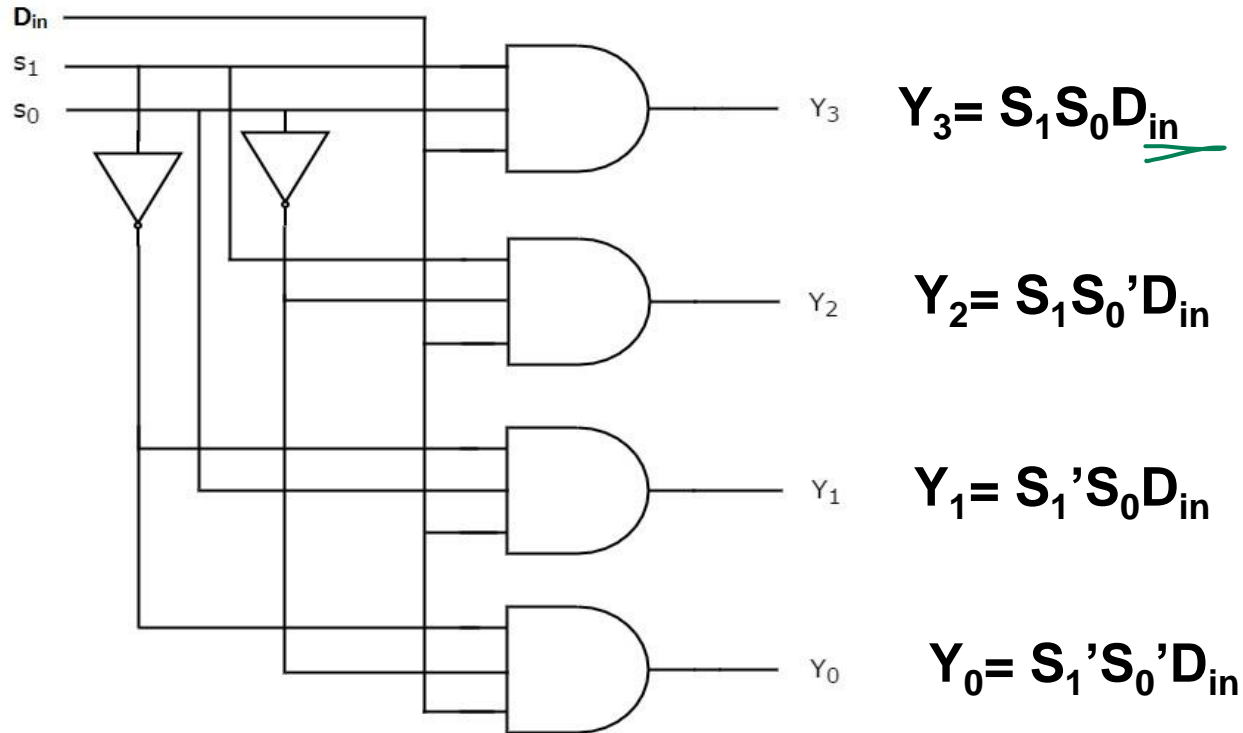

Multiplexer (as universal logic gate)

- Multiplexer is also act as universal logic gate.
- It means that any of the logic circuit/gate can be implemented with the help of multiplexer.

h

Implementation using MUX (Method 1)

- Example: Design 2-input OR gate with the help of MUX.


- The Boolean equation for OR gate is-

$$F(A,B) = A+B$$

- First choose the size of MUX-

- No. of select lines (n) = No. of variables in given Boolean function
 - No. of select lines (n) = 2 (A,B)
 - No. of inputs (2^n) = 4
 - It requires 4:1 MUX to implement OR gate

Implementation using MUX (Method 1)

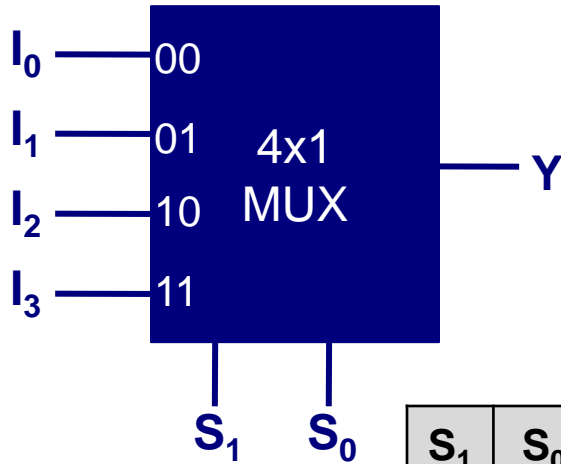


Function
Table
of MUX

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

$$F(A,B) = A+B$$


Truth Table
of OR

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

 

Implementation using mux (Method 1)

■ $F(A,B,C) = \sum m(1,3,5,6)$

 

Implementation using MUX (Method 2)


- Example: Design 2-input OR gate with the help of 2:1 MUX.

- The Boolean equation for OR gate is-

$$F(A,B) = A+B$$

- First choose the size of MUX-
 - No. of select lines (n) = No. of variables - 1
 - No. of select lines (n) = 2 - 1 = 1
 - No. of inputs (2^n) = 2
 - It requires 2:1 MUX to implement OR gate

Implementation using MUX (Method 2)

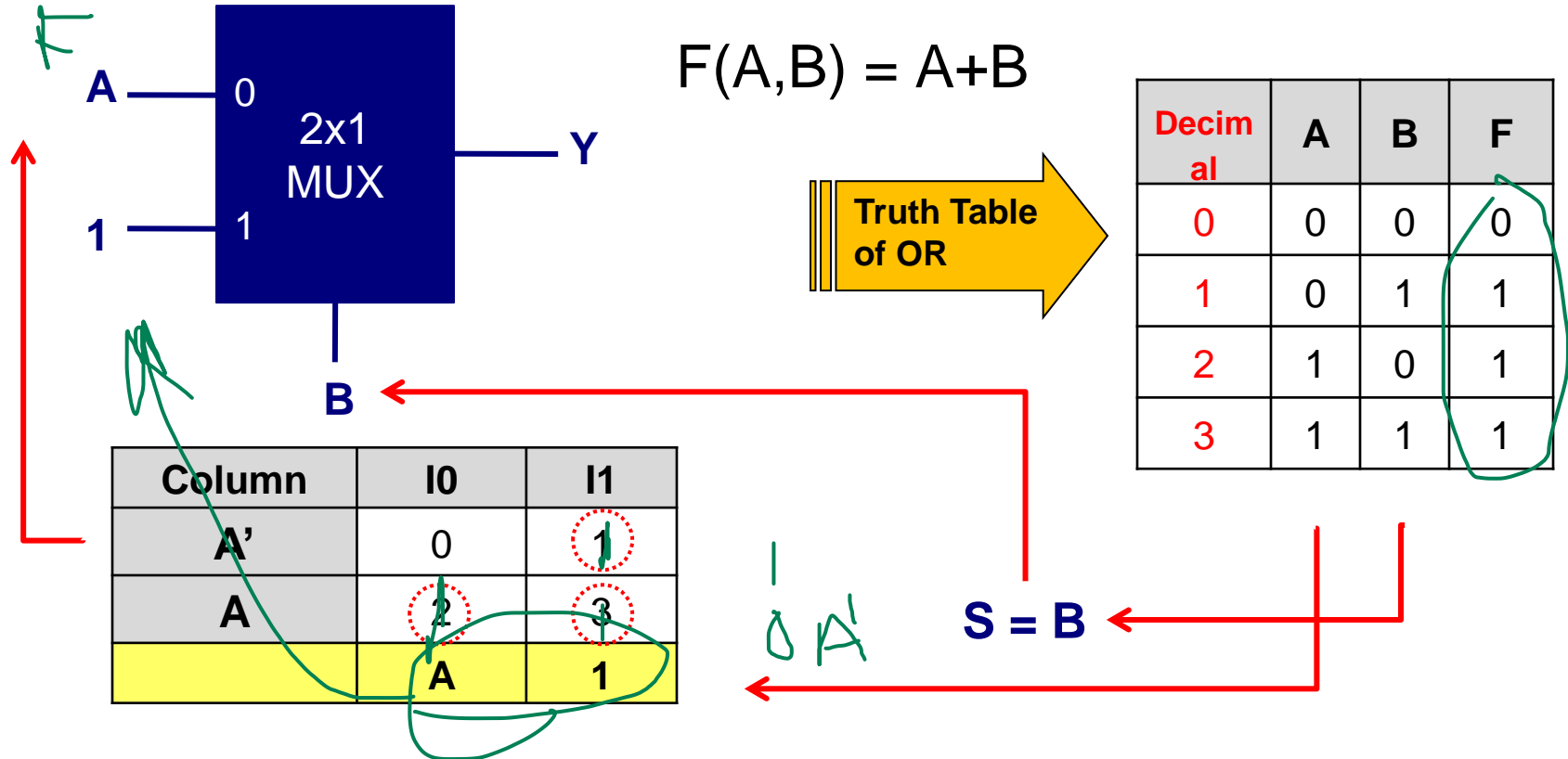

Implementation using mux (Method 2)

$$F(A,B,C) = \sum m(1,3,5,6)$$

Minterm	A	B	C	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

Fig. 3.57 (a) Truth table

	D ₀	D ₁	D ₂	D ₃	
\bar{A}	0	①	2	③	Row 1
A	4	⑤	⑥	7	Row 2
	0	1	A	\bar{A}	

Fig. 3.57 (c) Implementation table

 


Fig. 3.57 (b) Multiplexer implementation

Implementation using MUX (Method 2)


Design the following function by using MUX

$$F(A,B,C) = \Sigma m(0,4,5,7)$$


Solution: First choose the size of required MUX-

- No. of select lines (n) = No. of variables - 1
- No. of select lines (n) = 3 - 1 = 2
- No. of inputs (2^n) = 4
- It requires 4:1 MUX to implement the given function

Implementation using MUX (Method 2)

 

$$F(A,B,C) = \Sigma m(0,4,5,7)$$

 

Column	I0	I1	I2	I3
A'	0	1	2	3
A	4	5	6	7
	1	A	0	A

$$S_1 = B$$

$$S_0 = C$$

Decimal	A	B	C	F
0	0	0	0	1
1	0	0	1	0
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	0
7	1	1	1	1

Question

- Implement the following function using 8:1 Mux
 - $F(P,Q,R,S) = \sum m(0,1,3,4,8,9,15)$


Question

- Implement the following function using 8:1 Mux

□ $F(P,Q,R,S) = \sum m(0,1,3,4,8,9,15)$

	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
\bar{A}	①	①	2	③	④	5	6	7
A	⑧	⑨	10	11	12	13	14	⑮
	1	1	0	\bar{A}	\bar{A}	0	0	A

(a) Implementation table

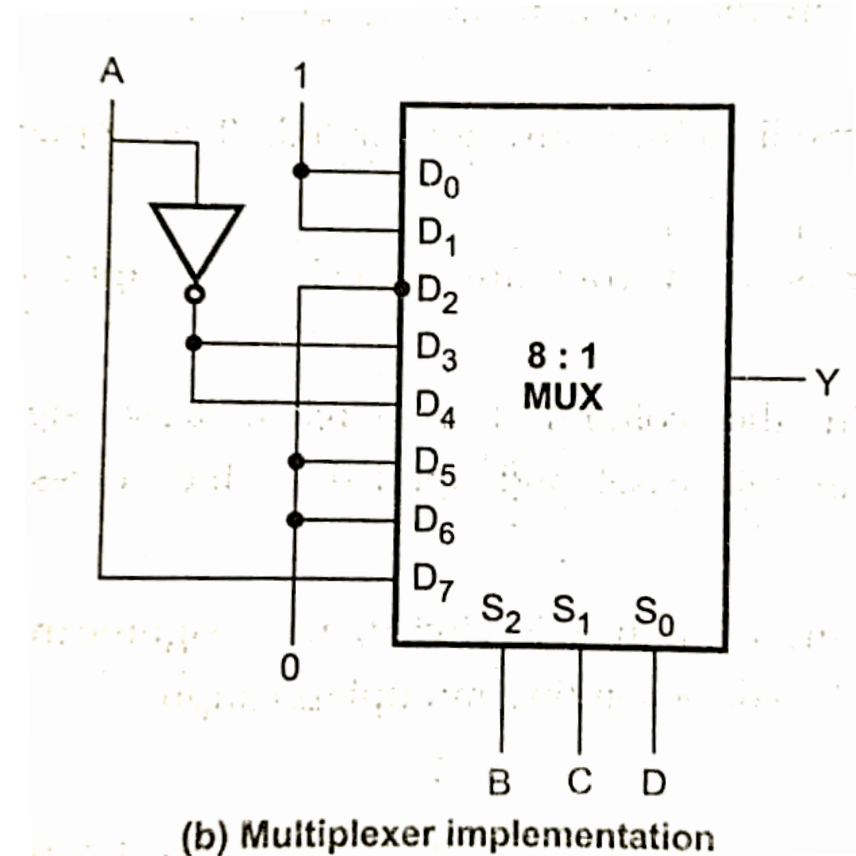

Question

- Implement the following function using 8:1 Mux
 - $F(A,B,C,D) = \sum m(0,2,6,10,11,12,13) + d(3,8,14)$


Question

- Implement the following function using 8:1 Mux

$$F(A,B,C,D) = \sum m(0,2,6,10,11,12,13) + d(3,8,14)$$


	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
\bar{A}	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15
	1	0	1	1	A	A	1	0

Here, don't cares are treated as 1s

 


Taking Don't care as 1
we have removed the
inverter for Abar

Decoder

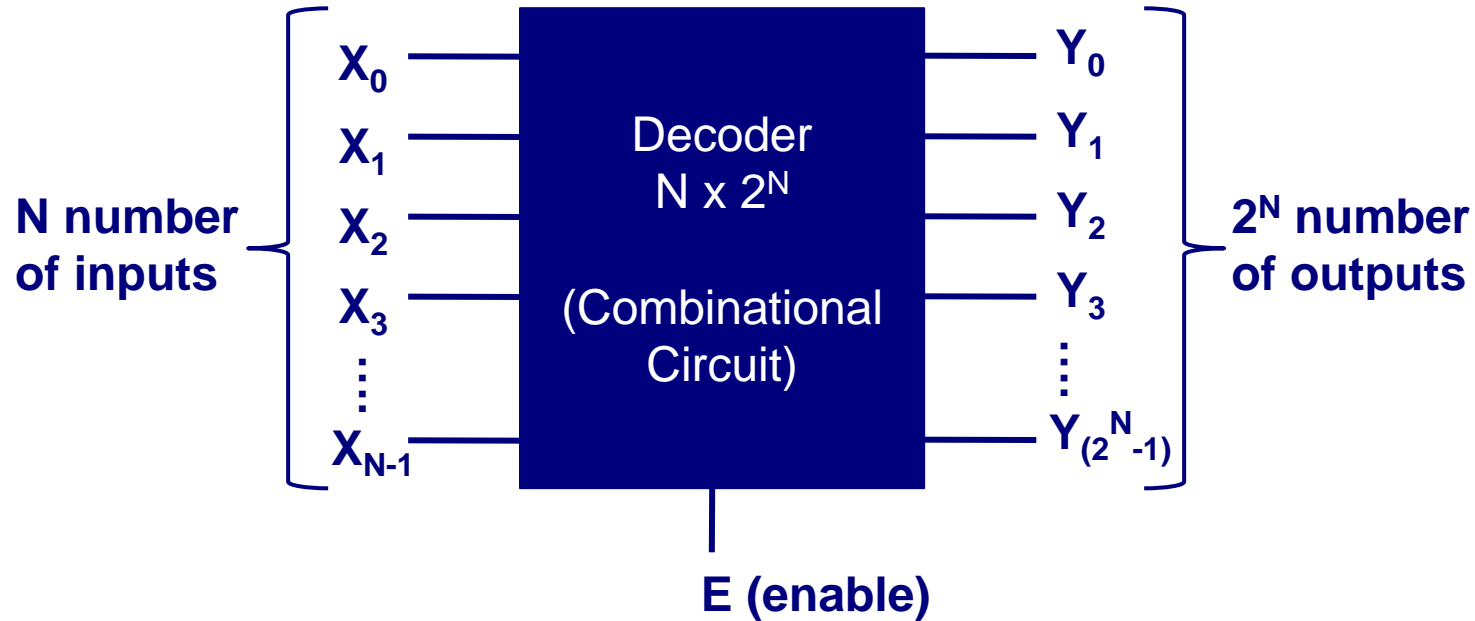

2x4 Decoder

 

$$Y_0 = EA'B'$$


$$Y_2 = EAB'$$

$$Y_1 = EA'B$$


$$Y_3 = EAB$$

E	A	B	Y ₀	Y ₁	Y ₂	Y ₃
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1


2x4 Decoder

 

3x8 Decoder

 


3x8 Decoder

 

E	A	B	C	Y ₀	Y ₁	Y ₂	Y ₃	Y ₄	Y ₅	Y ₆	Y ₇
0	X	X	X	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	0	0	0	0
1	0	0	1	0	1	0	0	0	0	0	0
1	0	1	0	0	0	1	0	0	0	0	0
1	0	1	1	0	0	0	1	0	0	0	0
1	1	0	0	0	0	0	0	1	0	0	0
1	1	0	1	0	0	0	0	0	1	0	0
1	1	1	0	0	0	0	0	0	0	1	0
1	1	1	1	0	0	0	0	0	0	0	1

3x8 Decoder

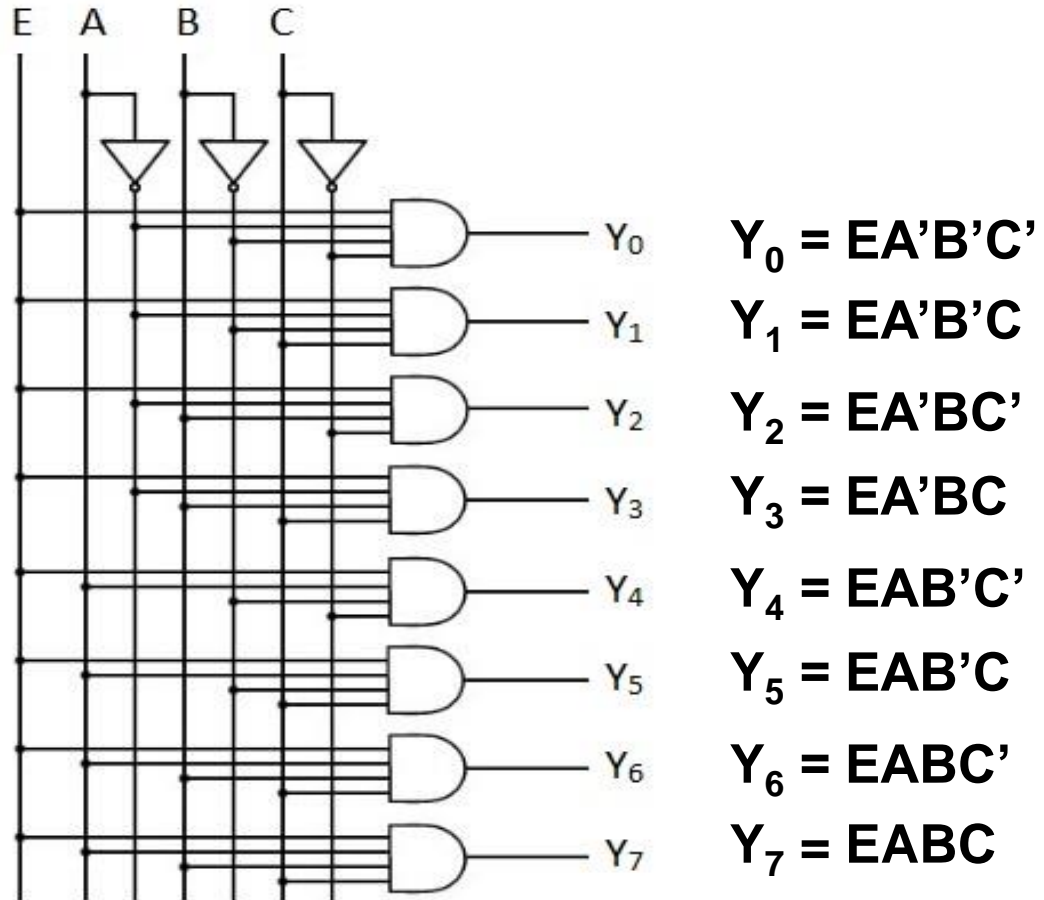

4 to 16 Decoder

In this section, let us implement **4 to 16 decoder using 3 to 8 decoders**. We know that 3 to 8 Decoder has three inputs A_2, A_1 & A_0 and eight outputs, Y_7 to Y_0 . Whereas, 4 to 16 Decoder has four inputs A_3, A_2, A_1 & A_0 and sixteen outputs, Y_{15} to Y_0


We know the following formula for finding the number of lower order decoders required.

$$\text{Required number of lower order decoders} = \frac{m_2}{m_1}$$


Substitute, $m_1 = 8$ and $m_2 = 16$ in the above formula.

$$\text{Required number of 3 to 8 decoders} = \frac{16}{8} = 2$$



4:16 Decoder using 3:8 Decoder

 

Encoder

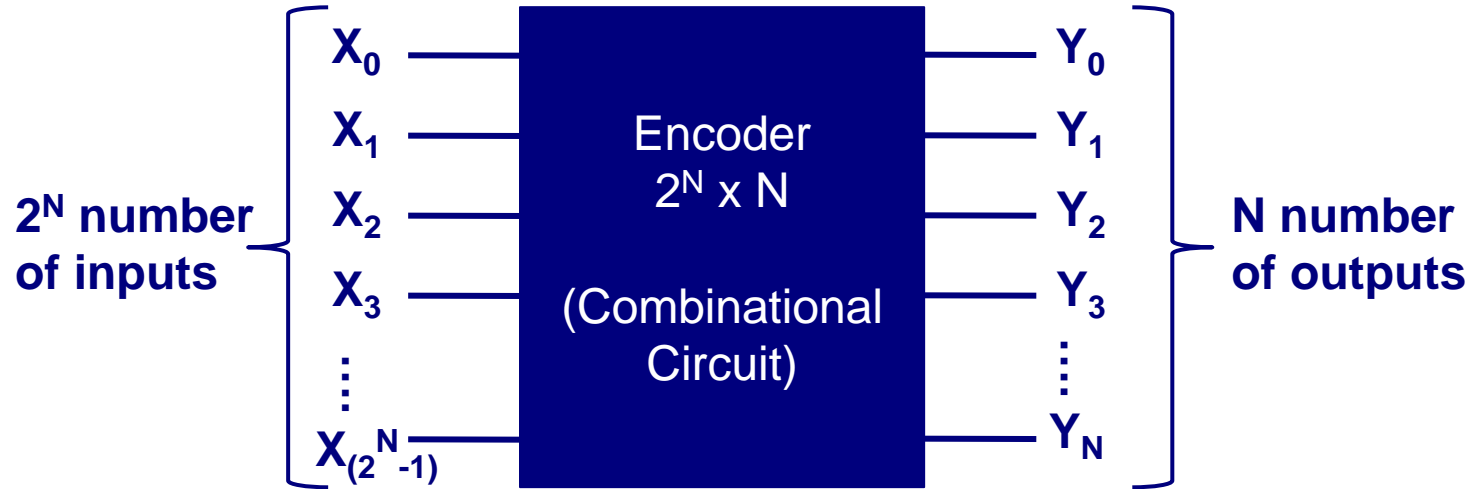

4x2 Encoder

  

D_0	D_1	D_2	D_3	Y_1	Y_0
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1
X	X	X	X	X	X

$$Y_0 = D_1 + D_3$$

$$Y_1 = D_2 + D_3$$

4x2 Encoder

K-map for
 Y_0 of 4x2
Encoder

D_2D_3 D_0D_1				
	0	1	3	2
	4	5	7	6
	12	13	15	14
	8	9	10	11

$$Y_0 = D_1 + D_3$$


4x2 Encoder

K-map for
 Y_1 of 4x2
Encoder


D_2D_3 D_0D_1				
	0	1	3	2
	4	5	7	6
	12	13	15	14
	8	9	10	11

$$Y_1 = D_2 + D_3$$

4x2 Encoder

 


8x3 Encoder (Octal to Binary)

 


$$Y_0 = D_1 + D_3 + D_5 + D_7$$

$$Y_1 = D_2 + D_3 + D_6 + D_7$$

$$Y_2 = D_4 + D_5 + D_6 + D_7$$

 [illegible]

8x3 Encoder (Octal to Binary)

 




Decoder (as universal logic gate)

- Decoder is also act as universal logic gate.
- It means that any of the logic circuit/gate can be implemented with the help of Decoder.


Implementation of Half adder using decoder

 - First, find out the no. of inputs required.



- So, half adder has 2 inputs.
- It means 2x4 decoder is required to design a half adder.

 Implementation of Half adder using decoder




Decimal	A	B	Sum	Carry
0	0	0	0	0
1	0	1	1	0
2	1	0	1	0
3	1	1	0	1

$$\text{Sum} = \Sigma m(1,2)$$


$$\text{Carry} = \Sigma m(3)$$

 Implementation of Half adder using decoder




Decoder (as universal logic gate)

 - Implement a full adder with the help of decoder.
 - First, find out the no. of inputs required.



- So, full adder has 3 inputs.
- It means 3x8 decoder is required to design a full adder.

 Implementation of full adder using decoder




$$\text{Sum} = \Sigma m(\underline{1,2,4,7})$$

$$\text{Carry} = \Sigma m(\underline{3,5,6,7})$$

Decimal	A	B	C	Sum	Carry
0	0	0	0	0	0
1	0	0	1	1	0
2	0	1	0	1	0
3	0	1	1	0	1
4	1	0	0	1	0
5	1	0	1	0	1
6	1	1	0	0	1
7	1	1	1	1	1

 Implementation of full adder using decoder





Thank You